

<b>R</b>	<b>A</b>	<b>2</b>	<b>1</b>											
----------	----------	----------	----------	--	--	--	--	--	--	--	--	--	--	--

**COLLEGE OF ENGINEERING & TECHNOLOGY,  
SRM INSTITUTE OF SCIENCE AND TECHNOLOGY  
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**

**Cycle Test – I**

**SET- C**

**Academic Year: 2021-2022 (EVEN SEM)**

**Program offered: B.Tech**

**Year / Sem : I/II**

**Course Code and Title: 18EES101J/ BASIC ELECTRICAL  
AND ELECTRONICS ENGINEERING**

**Maximum Marks: 25**

**Date and Time: 21/04/2022 and 12:30 pm to 01:20 pm**

**PART A (Answer all the questions)**


**3x4 MARKS=12 MARKS**

Learning Assessment (CLA 1)			
Levels	Level of Thinking	Weightage Required (%)	Weightage Provided(%)
1	Remember	40%	40%
	Understand		
2	Apply	60%	60%
	Analyze		


Q. No.	Questions	Refer ence to CO	Ref ere nce to PO	Bloom's Taxonomy	Mark s Allott ed	Marks Scored
1.	State Ohm's law and also list out its limitations.	CO1	1	Understand	4	
2.	A circuit consists of three resistors 3 $\Omega$ , 4 $\Omega$ and 6 $\Omega$ in parallel and a fourth resistor of 4 $\Omega$ in series. A battery of 12 V and an internal resistance of 6 $\Omega$ is connected across the circuit. Find the total current in the circuit and the terminal voltage across the battery.	CO1	1,2	Apply	4	
3.	Each phase of a three-phase alternator, generates a voltage of 3810.5 V and can carry a maximum current of 30 A. Find the line current, line voltage and total kVA capacity, if the alternator is connected in star.	CO1	1,2	Understand	4	

**PART B(Answer all the questions)**

**1x13 MARKS=13 MARKS**

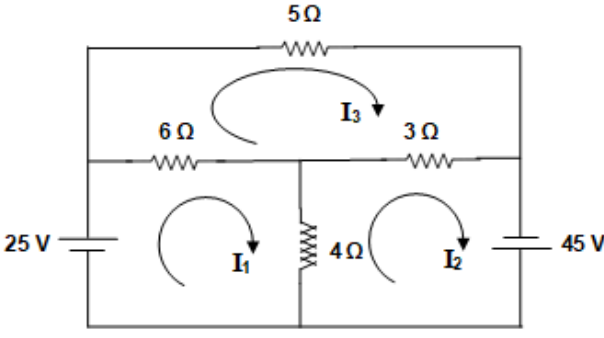Q. No.	Questions	Refer ence to CO	Refer ence to PO	Blooms Taxonomy	Marks Allotte d	Marks Scored
4a.	<p>Using Mesh analysis, find all the mesh currents in the given circuit shown below.</p> 	CO1	1,2	Apply	13	

**(OR)**

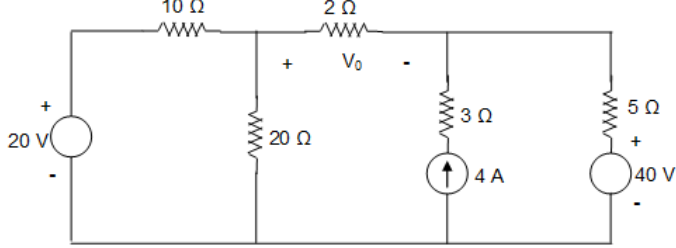4b.	<p>In the given circuit, find the voltage drop across the 2 ohms resistor by using super position theorem.</p> 	CO1	1,2	Apply	13	
-----	--	-----	-----	-------	----	--

Course Outcomes	Marks Allotted	Marks Scored
CO1	25	
CO2	-	-
CO3	-	-
CO4	-	-
CO5	-	-
CO6	-	-
Total	25	

**Total Marks Scored:**

**Signature of the Faculty**