

R	A	2	1											
----------	----------	----------	----------	--	--	--	--	--	--	--	--	--	--	--

**COLLEGE OF ENGINEERING & TECHNOLOGY,
SRM INSTITUTE OF SCIENCE AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING SET-C
Cycle Test – II**

Academic Year: 2021-2022 (EVEN SEM)
Program offered: B.Tech
Year / Sem : I/II
Course Code and Title: 18EES101J/ BASIC ELECTRICAL AND ELECTRONICS ENGINEERING
Maximum Marks: 50
Part A Duration: 20 mins [12.30-12.50 PM]

Learning Assessment (CLA 1)			
Levels	Level of Thinking	Weightage Required (%)	Weightage Provided(%)
1	Remember	40%	36%
	Understand		
2	Apply	60%	64%
	Analyze		
	Create		

PART A (Answer all the questions)

10x1 MARK=10 MARKS

Q. No.	Questions [BUBBLE (ROUND) THE CORRECT ANSWER, DO ROUGH WORK IN MAIN ANSWER SHEET]	Ref ere nce to CO	Refer ence to PO	Bloom's Taxonomy	Mark s Allott ed	Marks Scored
1.	According to Faraday's law of Induction ----- <ul style="list-style-type: none"> ○ Emf is induced in a conductor when it cuts the magnetic flux ○ Emf is induced in a conductor when it moves parallel to the magnetic field ○ Emf is induced in a conductor when it moves perpendicular to the magnetic field ○ Emf is induced in a conductor when it is just entering a magnetic field 	CO 2	1	Remember	1	
2.	Which is the following is true for a transformer? <ul style="list-style-type: none"> ○ Transformer is used to step down or up the AC voltages and currents ○ Transformer is used to step down or up the DC voltages and currents ○ Transformer converts DC to AC voltages ○ Transformer converts AC to DC voltages 	CO 2	1,	Remember	1	
3.	A single phase induction Motor is ----- <ul style="list-style-type: none"> ○ Self-starting with high torque ○ Self-starting with zero torque ○ Self-starting with low torque ○ Not self-starting 	CO 2	1	Understand	1	
4.	Starters are used in a DC motor because <ul style="list-style-type: none"> ○ Back emf of these motors is zero initially ○ These motors are not self-starting ○ These motors have high starting torque ○ It restricts the armature current as there is no back emf at starting 	CO 2	1,2	Understand	1	

5.	<p>The emf equation of DC generator is $E = \frac{\phi P}{ZNA}$</p> <ul style="list-style-type: none"> <input type="radio"/> $\frac{\phi P}{ZNA}$ <input type="radio"/> $\frac{\phi P * 60}{ZNA}$ <input type="radio"/> $\frac{\phi PA}{60NA}$ <input type="radio"/> $\frac{\phi PNZ}{60A}$ 	CO 2	1,2	Understand	1	
6.	<p>Which among the following is the function of a PN-junction diode?</p> <ul style="list-style-type: none"> <input type="radio"/> Condenser <input type="radio"/> Regulator <input type="radio"/> Amplifier <input type="radio"/> Rectifier 	CO 3	1,2	Understand	1	
7.	<p>The efficiency of a full wave rectifier is _____</p> <ul style="list-style-type: none"> <input type="radio"/> 50% <input type="radio"/> 46% <input type="radio"/> 70% <input type="radio"/> 81.2% 	CO 3	1,2	Understand	1	
8.	<p>Mixture preferred for filling around the earth electrode for effective earthing is -----</p> <ul style="list-style-type: none"> <input type="radio"/> paper-salt mixture <input type="radio"/> saw dust mixture <input type="radio"/> coal-salt mixture <input type="radio"/> lime –sand mixture. 	CO 3	1,2	Understand	1	
9.	<p>Which of the following is true for a common emitter biased BJT configuration?</p> <ul style="list-style-type: none"> <input type="radio"/> High voltage and current gain <input type="radio"/> High voltage and low current gain <input type="radio"/> Low voltage and high current gain <input type="radio"/> Low voltage and high current gain 	CO 3	1,2	Understand	1	
10.	<p>-----of the following terminals does not belong to the MOSFET?</p> <ul style="list-style-type: none"> <input type="radio"/> Drain <input type="radio"/> Gate <input type="radio"/> Base <input type="radio"/> Source 	CO 3	1	Understand	1	

R	A	2	1											
----------	----------	----------	----------	--	--	--	--	--	--	--	--	--	--	--

**COLLEGE OF ENGINEERING & TECHNOLOGY,
SRM INSTITUTE OF SCIENCE AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING
Cycle Test – II**

Date : 03-06-2022

Academic Year: 2021-2022 (EVEN SEM)

SET-C

Program offered: B.Tech

Year / Sem : I/II

Course Code and Title: 18EES101J/ BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

Maximum Marks: 50

Duration: 1 hr 40 mins [12.30-2.10 PM]

PART B(Answer all the questions)

4x4 MARKS=16 MARKS

Q. No.	Questions	Refer ence to CO	Refer ence to PO	Blooms Taxonomy	Mar ks Allot ted	Marks Scored
11.	Derive the power and current equation for a pure capacitor circuit and also draw the phasor diagram for the same.	CO2	1,2	Apply	4	
12.	With neat diagram, explain the operation of unbiased positive clipper.	CO3	1	Apply	4	
13.	Discuss the working principle of transformer and application of core type transformer.	CO2	1	Understand	4	
14.	Design the wiring diagram for lighting 4 bulbs for a long corridor.	CO3	1,2,3	Understand	4	

PART C(Answer all the questions)

2x12 MARKS=24 MARKS

Q. No.	Questions	Refer ence to CO	Refer ence to PO	Blooms Taxonomy	Mark s Allott ed	Marks Scored
15. a	Elucidate with a neat diagram the working and operating principle of three phase induction motor and also brief on the rotor types in three phase induction motor.	CO2	1	Apply	12	
	(OR)					
15. b	Derive the RMS value, Average value peak and form factor for the wave form for sinusoidal shown.	CO2	1,2,3	Analyse	12	
16. a	Explain the working of NPN bipolar junction transistor on CE configuration and also. Describe the input and output characteristics.	CO3	1,2	Apply	12	
16. b	Describe the working principle of attraction and repulsion type moving iron type instruments. Also explain the drawback of MC over MI instruments	CO3	1,2	Apply	12	

Total Marks Scored:

Signature of the Faculty