

R	A	2	1											
---	---	---	---	--	--	--	--	--	--	--	--	--	--	--

COLLEGE OF ENGINEERING & TECHNOLOGY,
SRM INSTITUTE OF SCIENCE AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING
Cycle Test – I SET- B

Academic Year: 2021-2022 (EVEN SEM)

Program offered: B.Tech

Year / Sem : I/II

Course Code and Title: 18EES101J/ BASIC ELECTRICAL AND ELECTRONICS ENGINEERING



Maximum Marks: 25

Date and Time: 21/04/2022 and 08:00 am to 08:50 am

Learning Assessment (CLA 1)			
Levels	Level of Thinking	Weightage Required (%)	Weightage Provided(%)
1	Remember	40%	40%
	Understand		
2	Apply	60%	60%
	Analyze		


PART A (Answer all the questions)


3x4 MARK=12 MARKS

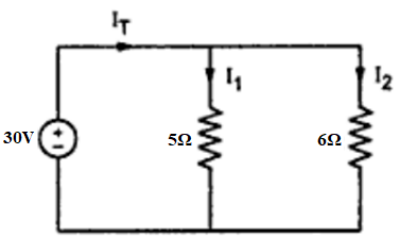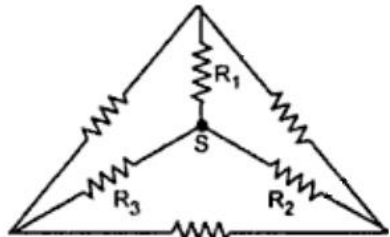Q. No.	Questions	Reference to CO	Reference to PO	Bloom's Taxonomy	Marks Allotted	Marks Scored
1.	a. Identify the current I_1 and I_2 in the given circuit using current division rule 	CO1	1	Understand	4	
2.	b. Give the current equation and the graph for a series R-L circuit State Thevenin's theorem. Illustrate briefly the procedure to arrive at its equivalent circuit.	CO1	1,2	Knowledge, Apply	4	
3.	Convert given star circuit to its equivalent delta form, if $R_1 = 2\Omega$, $R_2 = 3\Omega$ and $R_3 = 5\Omega$ 	CO1	1,2	Understand	4	

PART B (Answer all the questions)

1x13 MARKS=13 MARKS

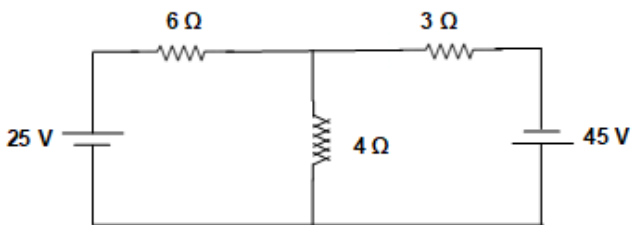Q. No.	Questions	Reference to CO	Reference to PO	Blooms Taxonomy	Marks Allotted	Marks Scored
4a.	Use mesh analysis to find current flowing through each resistor. Also find the power dissipated through 4Ω resistor 	CO1	1,2	Apply	13	

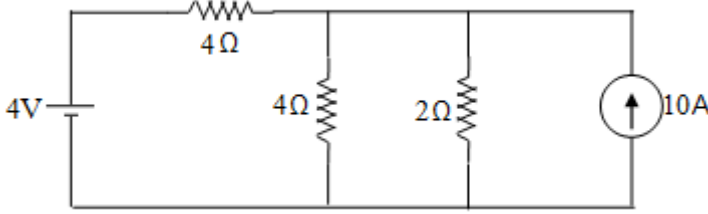(OR)						
4b.	Calculate the current through 2Ω resistor of the given circuit using superposition theorem 	CO1	1,2	Apply	13	

CO ASSESSMENT		
Course Outcomes	Marks Allotted	Marks Scored
CO1	25	
CO2	-	-
CO3	-	-
CO4	-	-
CO5	-	-
CO6	-	-
Total	25	

Total Marks Scored:

Signature of the Faculty