

R	A	2	1											
---	---	---	---	--	--	--	--	--	--	--	--	--	--	--

COLLEGE OF ENGINEERING & TECHNOLOGY,
SRM INSTITUTE OF SCIENCE AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Cycle Test – I

SET- D

Academic Year: 2021-2022 (EVEN SEM)

Program offered: B.Tech

Year / Sem : I/II

Course Code and Title: 18EES101J/ BASIC ELECTRICAL
AND ELECTRONICS ENGINEERING


Maximum Marks: 25

Date and Time: 21/04/2022 and 12:30 pm to 01:20 pm

Learning Assessment (CLA 1)			
Levels	Level of Thinking	Weightage Required (%)	Weightage Provided(%)
1	Remember	40%	40%
	Understand		
2	Apply	60%	60%
	Analyze		



PART A (Answer all the questions)

3x4 MARK=12 MARKS

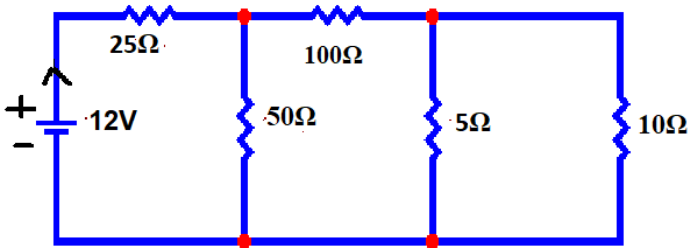Q. No.	Questions	Refer ence to CO	Ref ere nce to PO	Bloom's Taxonomy	Marks Allotte d	Marks Score d
1.a	What are active and passive elements?	CO1	1	Understand	2	
1.b	What is a lumped circuit?	CO1	1	Understand	2	
2.	<p>Find 'R' equivalent and current flowing due to a source of 12V for the circuit shown in Figure .</p> 	CO1	1,2	Apply	4	
3.	State and prove the maximum power transfer theorem.	CO1	1,2	Understand	4	

PART B(Answer all the questions)

1x13 MARKS=13 MARKS

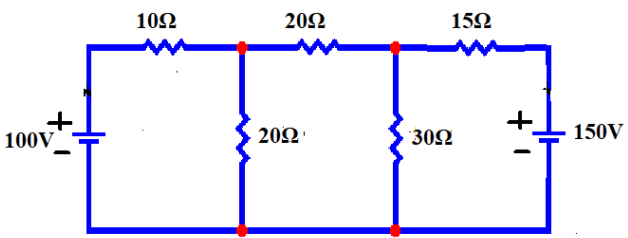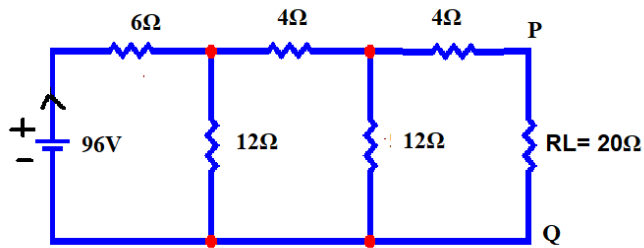Q. No.	Questions	Refer ence to CO	Refer ence to PO	Blooms Taxonomy	Marks Allotted	Mar ks Scor ed
4a.	<p>Using nodal analysis, Find all node voltage in the given circuit.</p> 	CO1	1,2	Apply	13	
(OR)						
4b.	<p>For the circuit. Determine the following:</p> <p>a) the open circuit emf at the load terminals PQ</p> <p>b) the Thevenin's resistance at PQ</p> <p>c) the load current</p> <p>d) load power</p> 	CO1	1,2	Apply	13	

Course Outcomes	Marks Allotted	Marks Scored
CO1	25	
CO2	-	-
CO3	-	-
CO4	-	-
CO5	-	-
CO6	-	-
Total	25	

Total Marks Scored:

Signature of the Faculty